

# 04835370 人工智能芯片设计导论 Fall 2023 Memory & Arithmetic

燕博南





- Memory
- Arithmetic Unit






Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E <sup>2</sup> PROM	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM	FLASH  RRAM  MRAM  PCM	

# **Memory Spatial Abstraction**



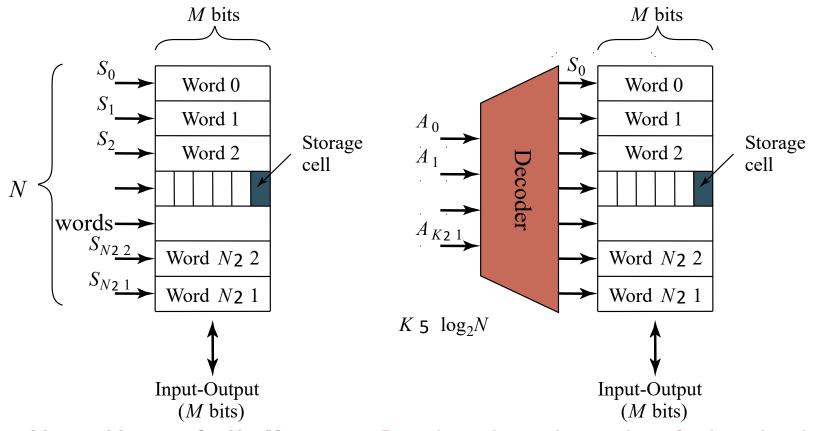


**Too many select signals:** N words == N select signals

Intuitive architecture for N x M memory Decoder reduces the number of select signals  $K = log_2 N$ 



# **Memory Timing Behavior**




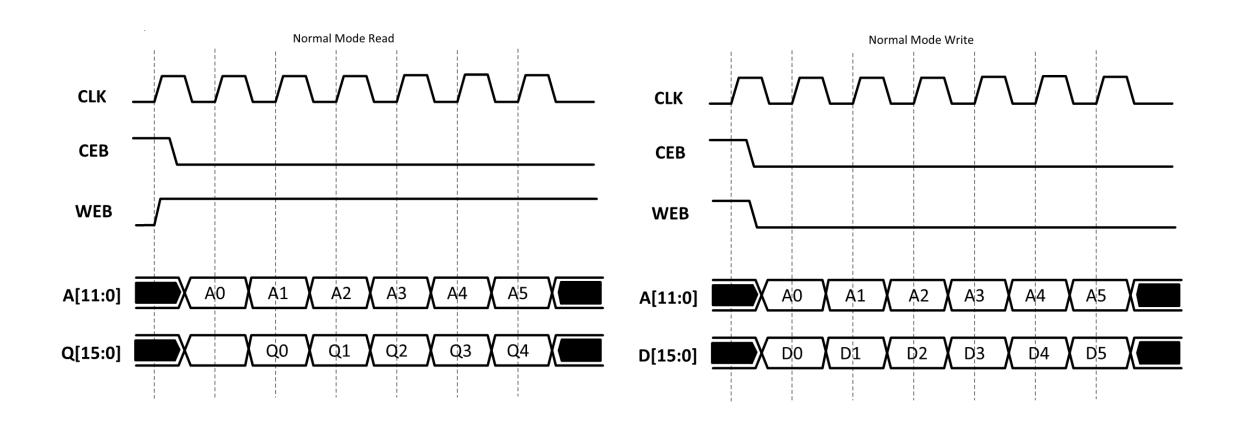


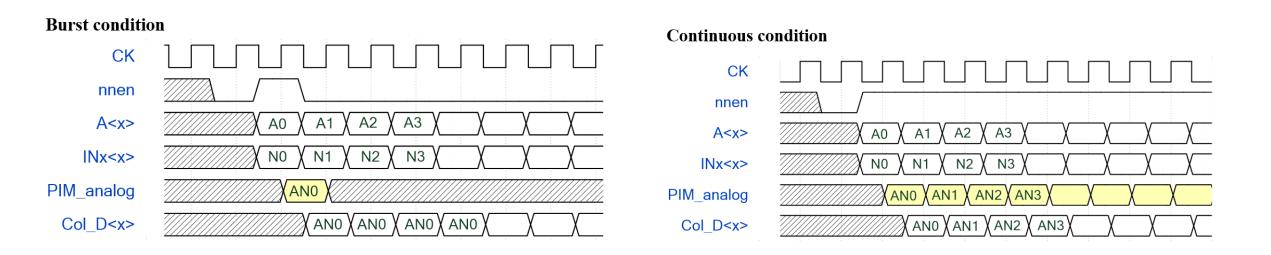
### Memory Timing Behavior / Compute-In-Memory







- Add additional (compute mode) inputs
- Perhaps additional address bits



#### **Memory Architecture**



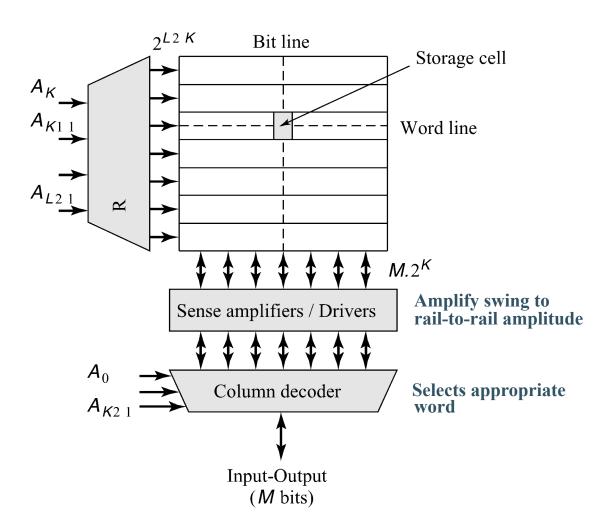

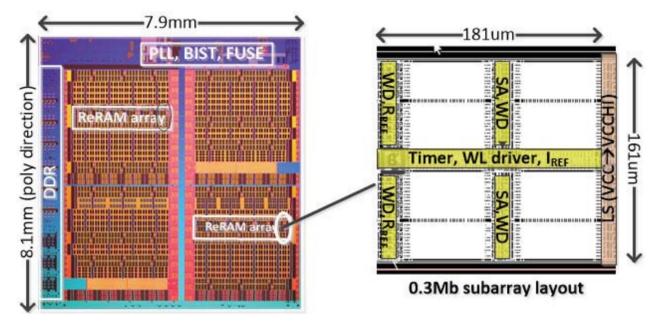


#### How it can achieve large capacity?

Jain, Pulkit, et al. "13.2 A 3.6 Mb 10.1 Mb/mm 2 embedded non-volatile ReRAM macro in 22nm FinFET technology with adaptive forming/set/reset schemes yielding down to 0.5 V with sensing time of 5ns at 0.7 V." 2019 IEEE International Solid-State Circuits Conference-(ISSCC). IEEE, 2019.



### **Memory Address**



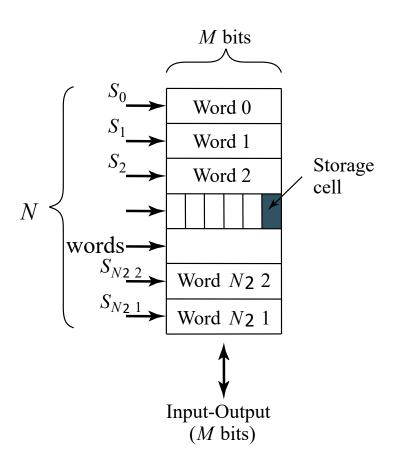

Each memory I/O bit width is 128bit

For 1Mb memory, what is the range of memory address?

1Mb/128b =  $(2^{20} \text{ bit})/(2^7 \text{ bit})$ =  $2^{13}$ 


13-wire address is necessary



#### A Practical DRAM Product



Figure 3: 1 Gig x 8 Functional Block Diagram

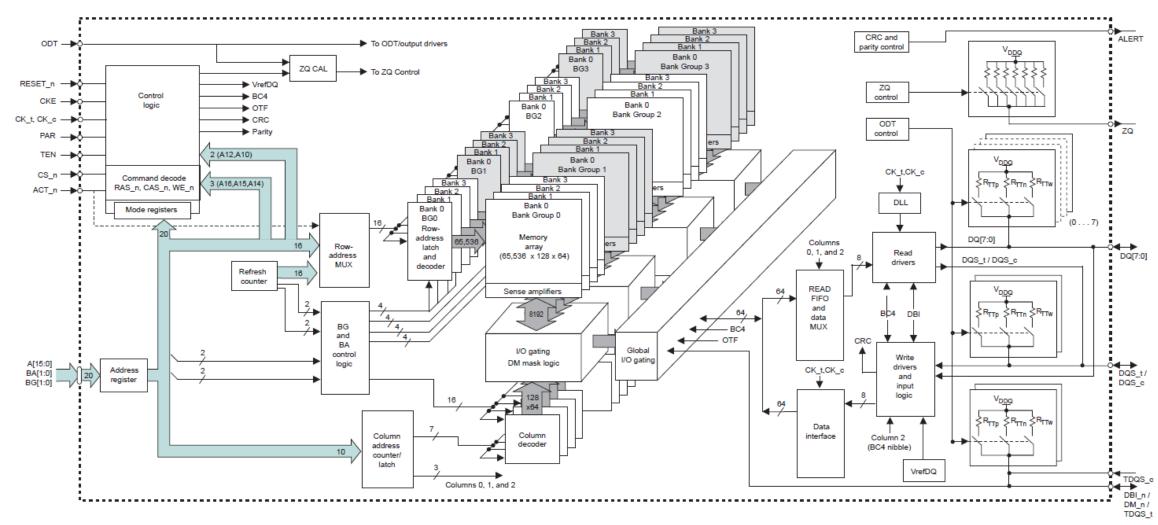


Source: Micron




### Memory Behavioral Model



https://bonany.gitlab.io/pis/

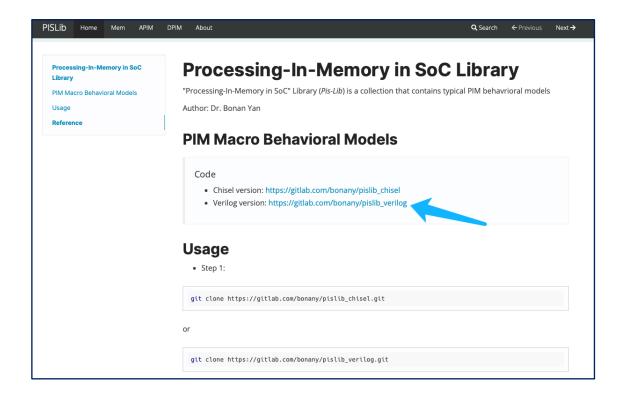

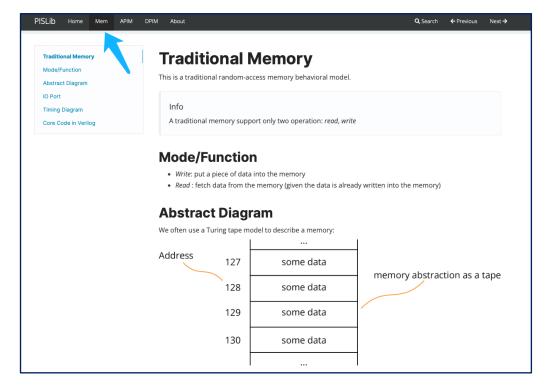






- Memory
- Arithmetic Unit
  - Number Systems
    - Integer
    - Fixed-Point
    - Floating-Point
  - Arithmetic
  - Circuits & Implementation

Numbers Arithmetic Circuits



### Why We Need to Introduce Arithmetic



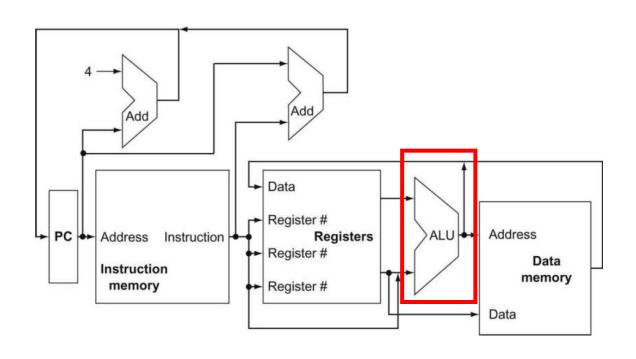

- Arithmetic Logic Unit (ALU): heart of von Neumann architecture
- Deal with various precisions: decimals, fractions, integers, ...




# Part 1

**Unsigned Integers** 



# **Number System of Digital Computers**



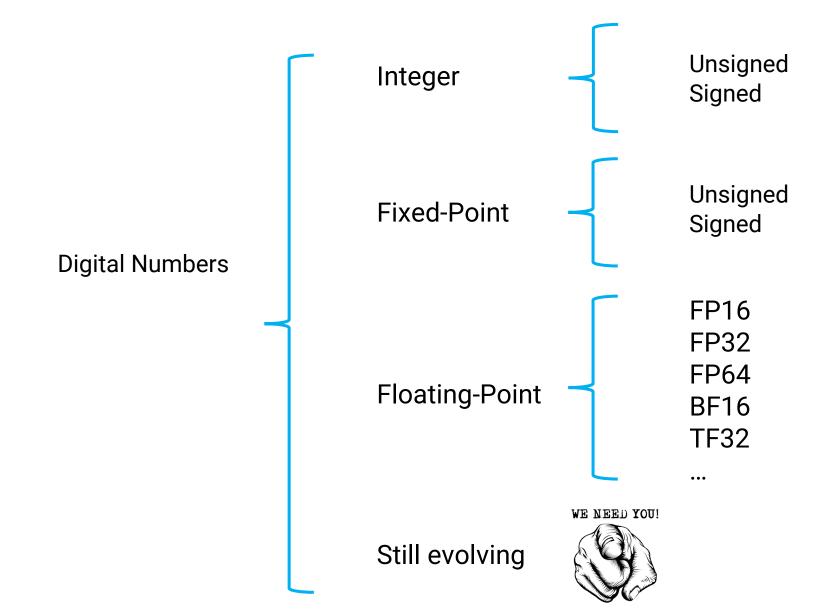




#### **Unsigned Integer**



Numbers Arithmetic Circuits

Unsigned INT32

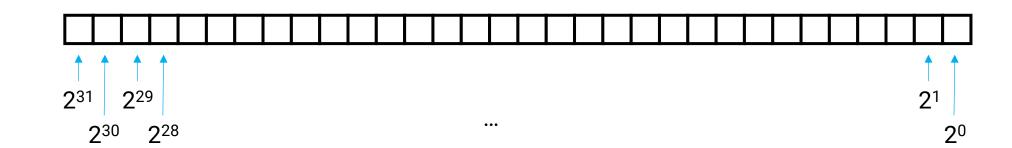

Significance:

- INT16, INT8, ...
- Example:

32'd7 (=32'h0000\_0007) 8'b1100\_1101 (=8'hCD) Recommend tool: programmer's calculator

## **Unsigned Integer Arithmetic - Add & Subtract**




INT4 as example:

Add: 
$$4'd7 + 4'd5 = 4'd12$$



Subtract: 4'd12 - 4'd5 = 4'd7

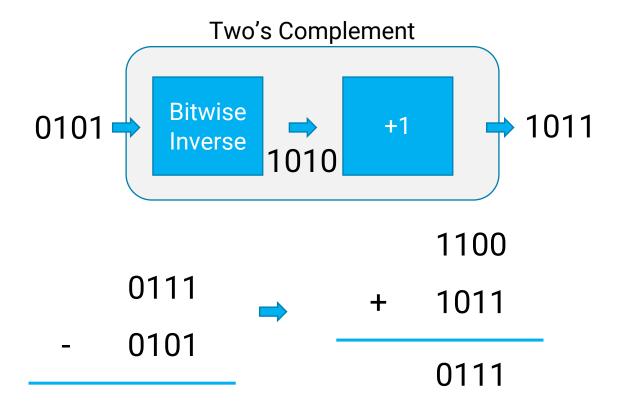

## Unsigned Integer Arithmetic - Multiply & Divide



Numbers Arithmetic Circuits

• INT4 as example:

Multiply: 
$$4'd3 * 4'd5 = 4'd15$$



### **Unsigned Integer Circuits - Adder**



**Numbers** 

> Arithmetic

Circuits


Half-Adder

$$C_{out}$$
 $A$ 
 $B$ 
 $C$ 
 $S$ 

A	В	<b>C</b> out	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$
$$C_{\text{out}} = A \cdot B$$

Full-Adder

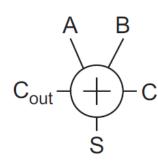

Α	В	С	G	P	K	<b>C</b> out	S
0	0	0	0	0	1	0	0
Ü	O	1	Ŭ	O	1	0	1
0	1	0	0	1	0	0	1
Ü	1	1				1	0
1	0	0	0	0 1	1 0	0	1
1		1				1	0
1	1	0	1	0	0	1	0
1	1	1	1	J	Ü	1	1

$$S = A\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}\overline{B}C + ABC$$

$$= (A \oplus B) \oplus C = P \oplus C$$

$$C_{\text{out}} = AB + AC + BC$$

$$= AB + C(A + B)$$

$$= \overline{A}\overline{B} + \overline{C}(\overline{A} + \overline{B})$$

$$= MAJ(A, B, C)$$


## **Unsigned Integer Circuits - Adder (Cont.)**



**Numbers** 

> Arithmetic

Circuits

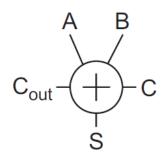

$$S = A\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}\overline{B}C + ABC$$


$$= (A \oplus B) \oplus C = P \oplus C$$

$$C_{\text{out}} = AB + AC + BC$$

$$= AB + C(A + B)$$

$$= \overline{AB} + \overline{C}(\overline{A} + \overline{B})$$

$$= MAJ(A, B, C)$$

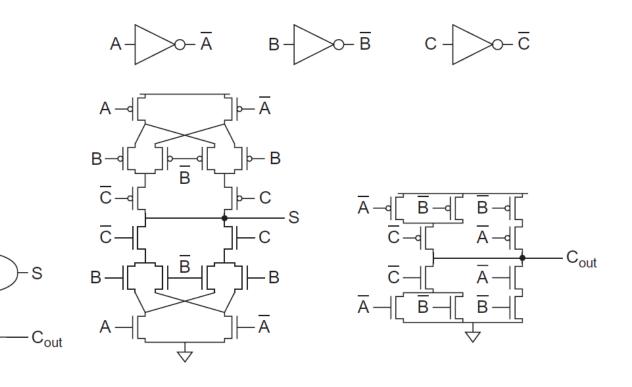


### **Unsigned Integer Circuits - Adder (Cont.)**



Numbers

> Arithmetic

Circuits

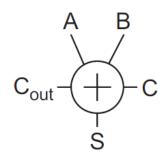

$$S = A\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}\overline{B}C + ABC$$

$$= (A \oplus B) \oplus C = P \oplus C$$


$$C_{\text{out}} = AB + AC + BC$$

$$= AB + C(A + B)$$

$$= \overline{AB} + \overline{C}(\overline{A} + \overline{B})$$

$$= MAJ(A, B, C)$$

#### Improved:

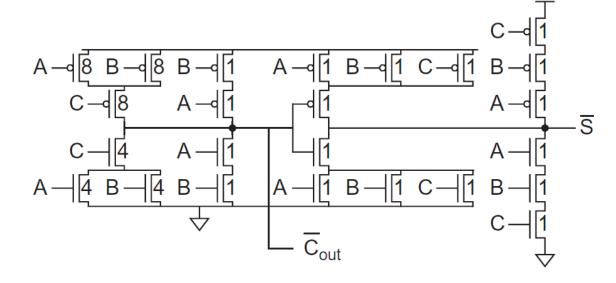

$$S = ABC + (A + B + C)\overline{C}_{out}$$

Idea behind:

Reuse Cout compute circuits to obtain both S




### **Unsigned Integer Circuits - Adder (Cont.)**




Numbers A

Arithmetic

Circuits

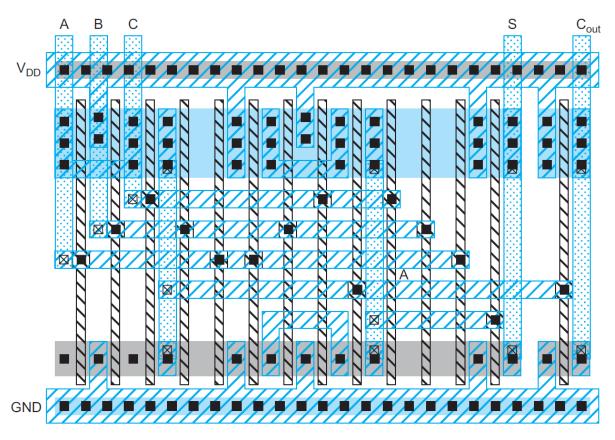

#### Improved:

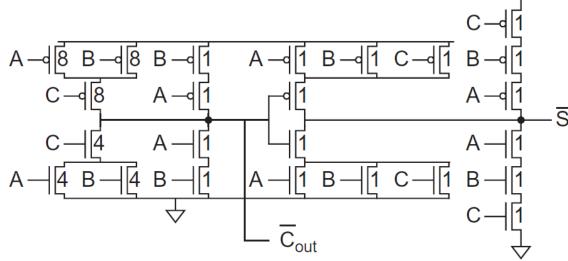

$$S = ABC + (A + B + C)\overline{C}_{out}$$

Idea behind:

Reuse Cout compute circuits to obtain both S




### Adder Family - Carry-Ripple Adder



Numbers

> Arithmetic

Circuits

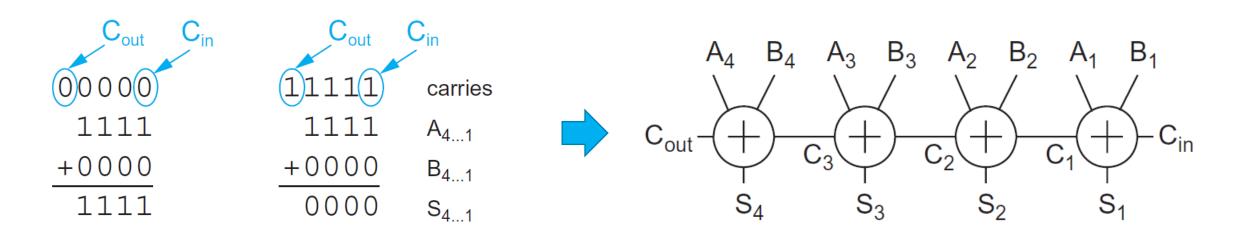


Natural & Intuitive However, carry propagation path too long

# Adder Family - Carry-Ripple Adder



Numbers Arithmetic Circuits

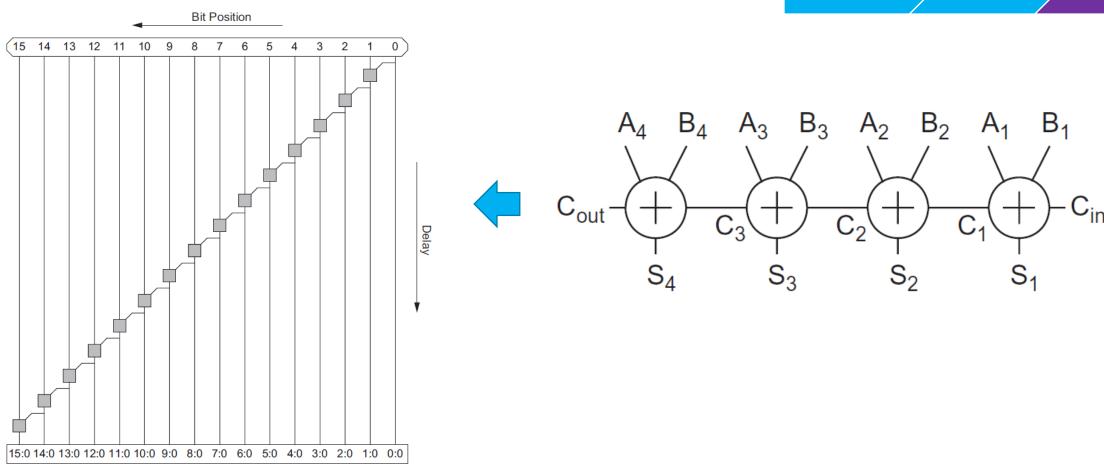

Weste, Neil HE, and David Harris. CMOS VLSI design: a circuits and systems perspective. Pearson Education India, 2015.



# Adder Family - Carry-Skip Adder





Numbers

> Arithmetic


Circuits


Carry-Skip Adder

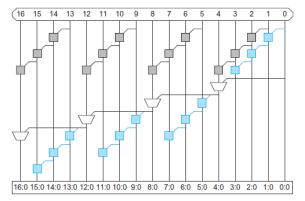

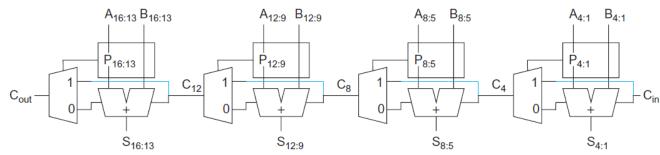

Carry-Lookahead Adder

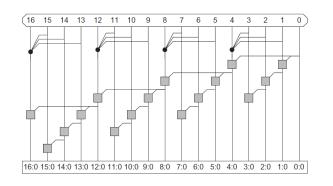

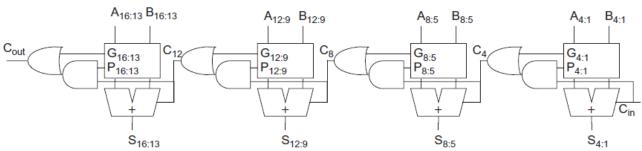

Idea Behind: Group and Divide!



## Adder Family - Big Family!


#### 和桌头等 PEKING UNIVERSITY

**Numbers** 


Arithmetic

Circuits


#### Tree Adder Family

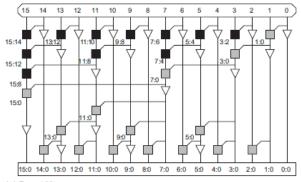


(a) Brent-Kung

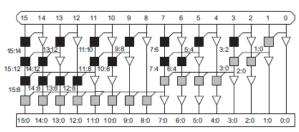


(b) Sklansky

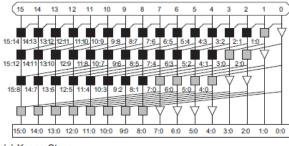


(c) Kogge-Stone

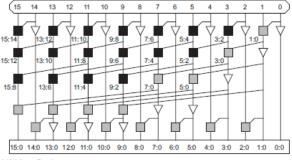

(d) Han-Carlson

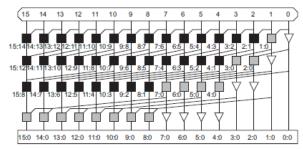


(e) Knowles [2,1,1,1]

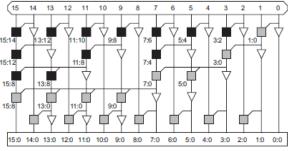


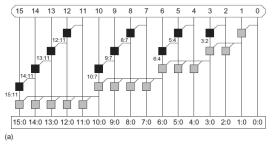(f) Ladner-Fischer

15 14 13 12 11 10 9 8 7 6 5 4 3 2 1 0 13:12 14:12 15:0 14:0 13:0 12:0 11:0 10:0 9:0 8:0 7:0 6:0 5:0 4:0 3:0 2:0 1:0 0:0



**Sarry-Incremental Adder** 

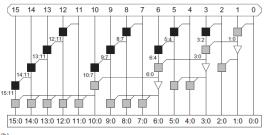


## Adder Family - Big Family! (Cont.)




#### Sparse Tree Adders


Numbers Arithmetic Circuits

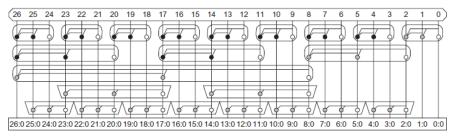


#### (a) Brent-Kung

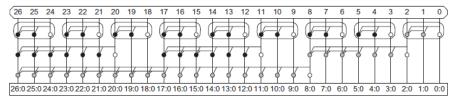



#### (b) Sklansky

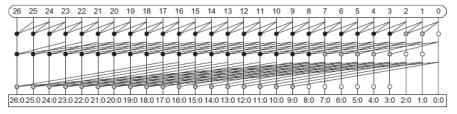


#### (c) Kogge-Stone

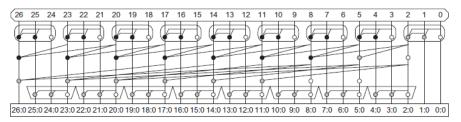

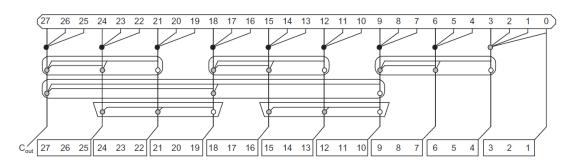

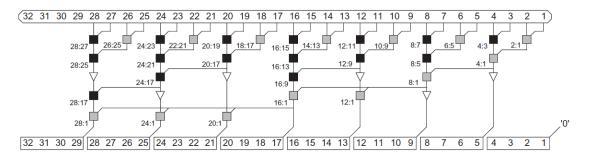


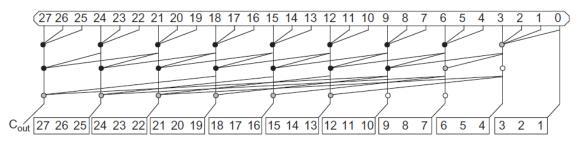

# Adder Family - Choose Wisely





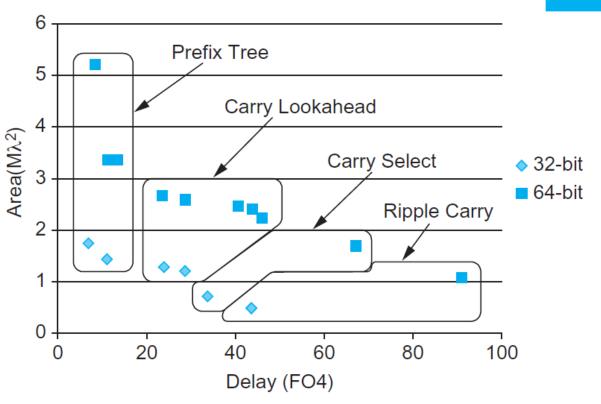

FO: Fan-Out

Everything has trade-off!

## **Unsigned Integer Circuits - Subtractor**




Numbers

Arithmetic

Circuits


$$C = A-B = A+ (-B)$$

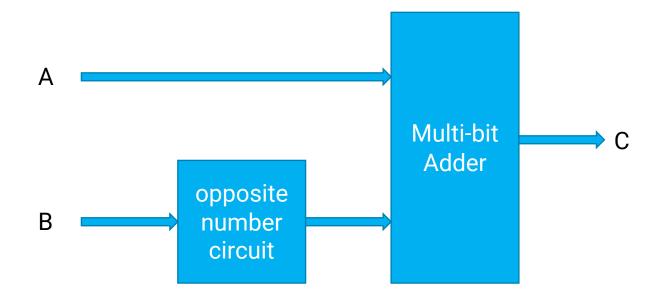

What is "opposite number circuit" though? [Save for a moment later]



Numbers Arithmetic Circuits

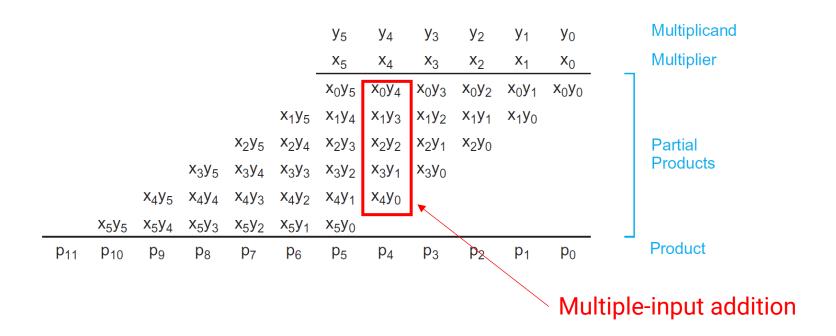

How do you implement it?

Yes! Adders!



Numbers

Arithmetic

 $C_3$   $S_3$ 

 $C_2 S_2$ 


 $X_{N...1}$   $Y_{N...1}Z_{N...1}$ 

n-bit CSA


Circuits

Carry-Save Adder (CSA) & "carry-save redundant format"

Example: Sum of 1011 1001 0011 1111

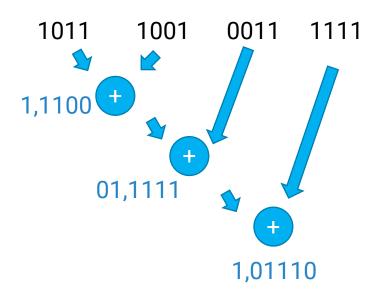

(Carry, Sum)

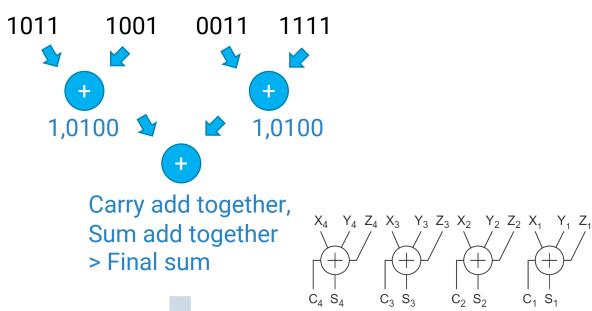







**Numbers** 

> Arithmetic


Circuits

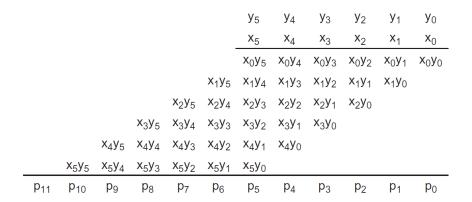

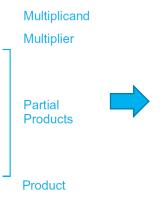

#### Partial Product: Single-bit multiplication is equivalent to "AND"

X	у	Partial product
0	0	0
0	0	0
1	0	0
1	1	1

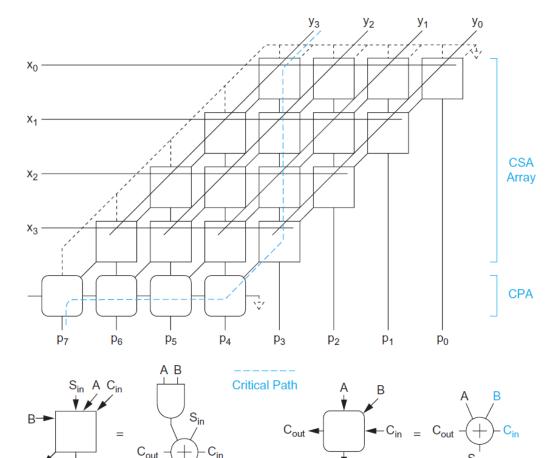







Numbers Arithmetic C

Circuits

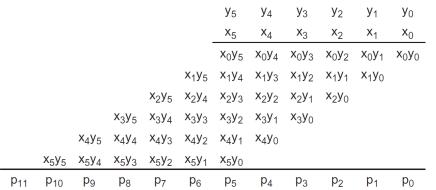


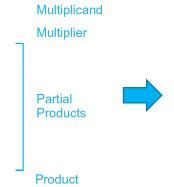

#### Partial Product: Single-bit multiplication is equivalent to "AND"

X	у	Partial product
0	0	0
0	0	0
1	0	0
1	1	1



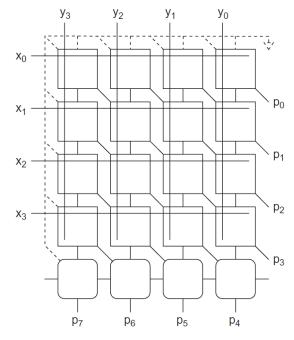

$$S_{\text{in}} \land C_{\text{in}}$$

$$S_{\text{in}} \land C_{\text{in}}$$

$$C_{\text{out}} \land C_{\text{in}}$$


### **Unsigned Integer Circuits - Divider**




Numbers

> Arithmetic

Circuits

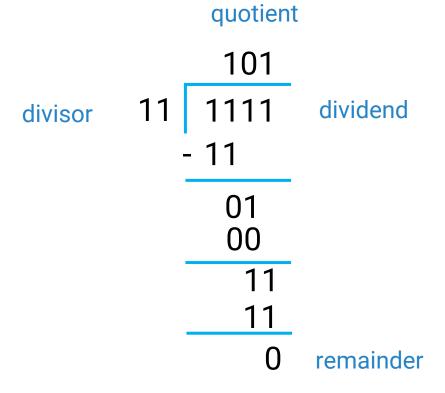

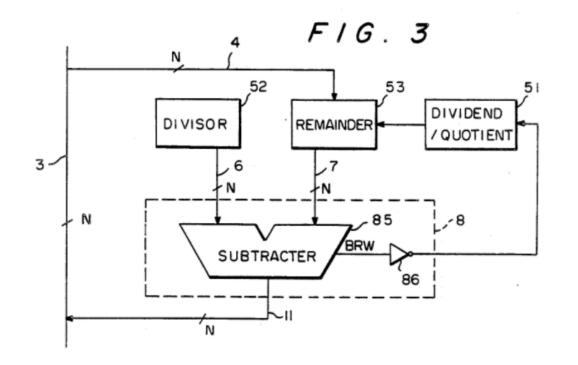

Yamahata, Hitoshi. "Integer division circuit provided with a overflow detector circuit." U.S. Patent No. 4,992,969. 12 Feb. 1991.



# Part 2

Signed Integers




## Signed Integer



Numbers Arithmetic Circuits

Signed INT32

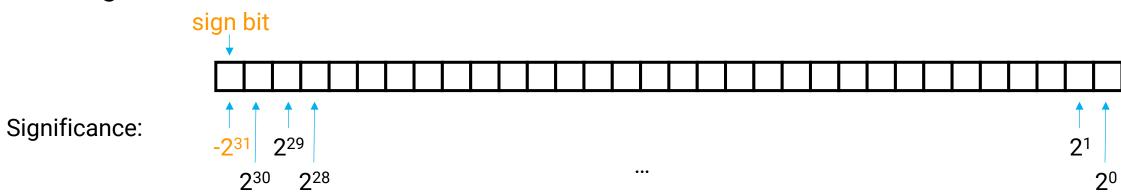

- INT16, INT8, ...
- Example:

-32'd7 (=32'hff\_ff\_ff\_f9) 8'b0100\_1101 (=8'hCD)

Signed Bit	Meaning
0	Positive
1	Negative

A Useful Tool: Cryptii



### **Signed Integer**



Problem: What is the range of signed vs. unsigned integers?


Numbers Arithmetic Circuits

For UINTn: 0~2<sup>n</sup>-1

For INTn:  $-2^{n-1} \sim 2^{n-1}-1$ 

# 
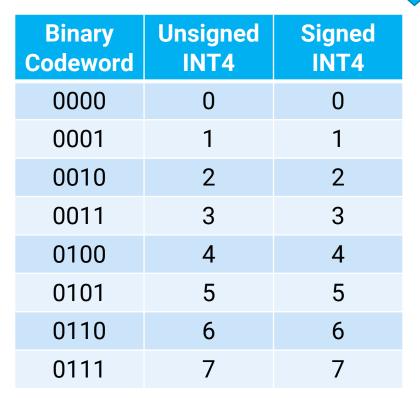
#### Here is the answer of "opposite number circuits"!




Binary Codeword	Unsigned INT4	Signed INT4
1000	8	-8
1001	9	-7
1010	10	-6
1011	11	-5
1100	12	-4
1101	13	-3
1110	14	-2
1111	15	-1


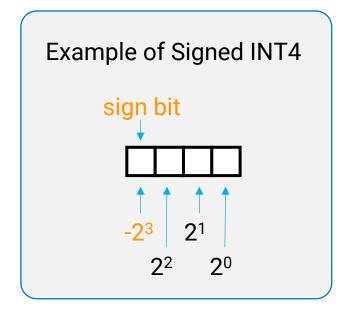
### Signed Integer - Two Types of Shift



- Verilog HDL supports 2 types of shift:
- Logic Shift Operators (<<, >>)
- Arithmetic Shift Operators (<<<, >>>)



- Numbers Arithmetic Circuits
- Logic shift >> <<: filling with zeros</li>
- 3'b100 >> 1'd1 gives 3'b010
- 3'b101 >> 1'd1 gives 3'b010
- 3'b101 << 1'd2 gives 3'b100

Not really stable rule: <<1 : multiply 2; >>1: divided by 2

- Arithmetic shift:
  - <<: Shift left specified number of bits, filling with zero.
  - >>>: Shift right specified number of bits, fill with value of sign bit if expression is signed, othewise fill with zero.



### Signed Integer - Two Types of Shift



Verilog HDL supports 2 types of shift:

•	Logic Shift Operators	(<<, >>)	)
---	-----------------------	----------	---

Arithmetic Shift Operators (<<<, >>>)

Binary Codewor	d Unsigned INT4	Signed INT4
1000	8	-8
1001	9	-7
1010	10	-6
1011	11	-5
1100	12	-4
1101	13	-3
1110	14	-2
1111	15	-1

4'b1110 >>> 1'd1 gives 4'b1111 4'b0110 >>> 1'd1 gives 4'b0011

- Numbers Arithmetic Circuits
- Logic shift >> <<: filling with zeros</li>
- 3'b100 >> 1'd1 gives 3'b010
- 3'b101 >> 1'd1 gives 3'b010
- 3'b101 << 1'd2 gives 3'b100

Not really stable rule: <<1: multiply 2; >>1: divided by 2

- Arithmetic shift:
  - <<: Shift left specified number of bits, filling with zero.
  - >>>: Shift right specified number of bits, fill with value of sign bit if expression is signed, othewise fill with zero.



# Part 3 About Fraction

Fixed-Point




### **Fixed-Point Number**



Numbers Arithmetic Circuits

• Fixed32

Significance:

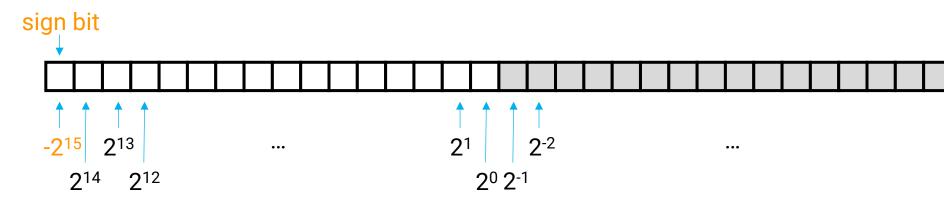

• Example:

$$(1.10)_2 = (1*2^0+1*2^{-1}+0*2^{-2})_{10} = (1.50)_{10}$$

Signed Bit	Meaning
0	Positive
1	Negative

### **Fixed-Point Number**



Arithmetic Just Works the Same Way!

**Numbers** Arithmetic Circuits

Verilog HDL does not support fixed-point natively




# Part 4

Floating-Point



Numbers Arithmetic Circuits

• FP32

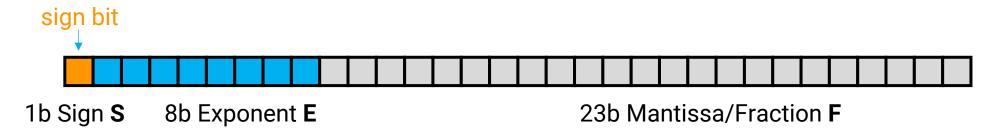


### Meaning:

Exponent	Fraction	Object	Value
0	0	0	
0	Nonzero	Denormalized number	$(-1)^{\mathbf{S}} \times (0.\mathbf{F}) \times 2^{\mathbf{E}-\mathbf{B}}$
Nonzero	Anything	Floating-point number	$(-1)^{\mathbf{S}} \times (1.\mathbf{F}) \times 2^{\mathbf{E}-\mathbf{B}}$
All "1"	0	infinity	
All "1"	Nonzero	NaN (not a number)	

1b Sign **S** 



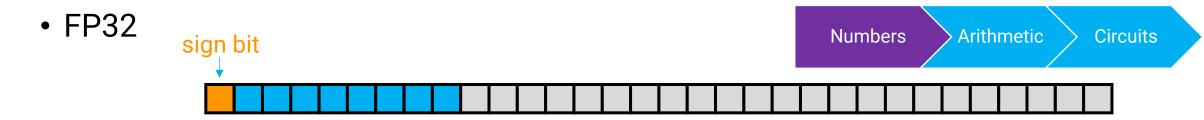

23b Mantissa/Fraction F

Exponent	Fraction	Object	Value
0	0	0	
0	Nonzero	Denormalized number	$(-1)^{S}\times(0.F)\times2^{E-B}$
Nonzero	Anything	Floating-point number	$(-1)^{S}\times(1.F)\times2^{E-B}$
All "1"	0	infinity	
All "1"	Nonzero	NaN (not a number)	

$$S=1$$
,  $E=0$ ,  $F=0$ , what is the value?  $-0=0$ 

8b Exponent E





• FP32

Numbers Arithmetic Circuits

Exponent	Fraction	Object	Value
0	0	0	
0	Nonzero	Denormalized number	$(-1)^{S} \times (0.F) \times 2^{1-B}$
Nonzero	Anything	Floating-point number	$(-1)^{S}\times(1.F)\times2^{E-B}$
All "1"	0	infinity	
All "1"	Nonzero	NaN (not a number)	

Туре	Sign	Exponent	Exponent bias	significand	total
Half (IEEE 754-2008)	1	5	15	10	16
Single	1	8	<b>B</b> 127	23	32
Double	1	11	1023	52	64
Quad	1	15	16383	112	128

S=0, E=0, F=23'b10000\_00000\_00000\_0000 what is its decimal value?

$$(0.1)_2 \times 2^{-127} = 0.5 \times 2^{-127}$$





• FP32

Numbers	Arithmetic	Circuits	

Exponent	Fraction	Object	Value
0	0	0	
0	Nonzero	Denormalized number	$(-1)^{S} \times (0.F) \times 2^{1-B}$
Nonzero	Anything	Floating-point number	$(-1)^{\mathbf{S}} \times (1.\mathbf{F}) \times 2^{\mathbf{E}-\mathbf{B}}$
All "1"	0	infinity	
All "1"	Nonzero	NaN (not a number)	

Туре	Sign	Exponent	Exponent bias	significand	total
Half (IEEE 754-2008)	1	5	15	10	16
Single	1	8	<b>B</b> 127	23	32
Double	1	11	1023	52	64
Quad	1	15	16383	112	128

S=0, E=8'b127, F=23'b10000\_00000\_00000\_0000 what is its decimal value?

$$(1.1)_2 \times 2^{127-127} = 1.5$$





• Range

Numbers	Arithmetic	Circuits	

Exponent	Fraction	Object	Value
0	0	0	
0	Nonzero	Denormalized number	$(-1)^{S} \times (0.F) \times 2^{1-B}$
Nonzero	Anything	Floating-point number	$(-1)^{S} \times (1.F) \times 2^{E-B}$
All "1"	0	infinity	
All "1"	Nonzero	NaN (not a number)	





Range

Numbers	Arithmetic	Circuits	

Exponent	Fraction	Object	Value
0	0	0	
0	Nonzero	Denormalized number	$(-1)^{S} \times (0.F) \times 2^{1-B}$
Nonzero	Anything	Floating-point number	$(-1)^{\mathbf{S}} \times (1.\mathbf{F}) \times 2^{\mathbf{E}-\mathbf{B}}$
All "1"	0	infinity	
All "1"	Nonzero	NaN (not a number)	

Absolute Min: S=0, E=8'b0000\_0001, F=23'h0000\_0000:  $(1.00000000000000000000001)_2*2^{1-127}$ =1.17549435082e-38

#### Denormalized:





Numbers Arithmetic Circuits

### Add

```
123456.7 = 1.234567 * 10^5

101.7654 = 1.017654 * 10^2 = 0.001017654 * 10^5

Hence:

123456.7 + 101.7654 = (1.234567 * 10^5) + (1.017654 * 10^2)

= (1.234567 * 10^5) + (0.001017654 * 10^5)

= (1.234567 + 0.001017654) * 10^5

= 1.235584654 * 10^5
```

```
E=5; F=1.234567 (123456.7)

+ E=2; F=1.017654 (101.7654)

E=5; F=1.234567

+ E=5; F=0.001017654 (after shifting) Round-off error

E=5; F=1.235584654 (true sum: 123558.4654)
```

Actually, result is: e=5; s=1.235585 (final sum: 123558.5)

Try by yourself: (E=5, F=1.234567) + (E=-3, F=9.876543) = ??





Numbers Arithmetic Circuits

### Subtract

```
Try by yourself: (E=5, F=1.234571) - (E=5, 1.234567) = ??
```

```
E=5; F=1.234571
- E=5; F=1.234567
------
E=5; F=0.000004
E=-1; F=4.000000 (after rounding/normalization)
```

Change to normalized form of FP numbers





Numbers Arithmetic Circuits

### Multiply:

```
E=3; F=4.734612

× E=5; F=5.417242

E=8; F=25.648538980104 (true product)

E=8; F=25.64854 (after rounding)

E=9; F=2.564854 (after normalization)
```

**Exponent: Sum Operation** 

Mantissa: Multiply Operation

Don't forget normalization

• Divide:

**Exponent: Subtract Operation** 

Mantissa: Divide Operation

Don't forget normalization

Q: What if normalized number multiplies denormalized number?





Numbers Arithmetic Circuits

# **Incompleteness of Floating-Point Arithmetic**

May not associative:


May not distributive:


$$1234.567 + 45.67844 = 1280.245$$
 $1280.245 + 0.0004 = 1280.245$ 
but
 $45.67840 + 0.00004 = 45.67844$ 
 $45.67844 + 1234.567 = 1280.246$ 

Arithmetic



#### Adder:

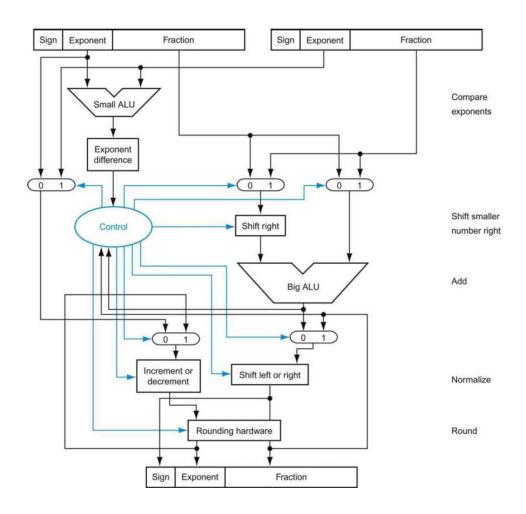


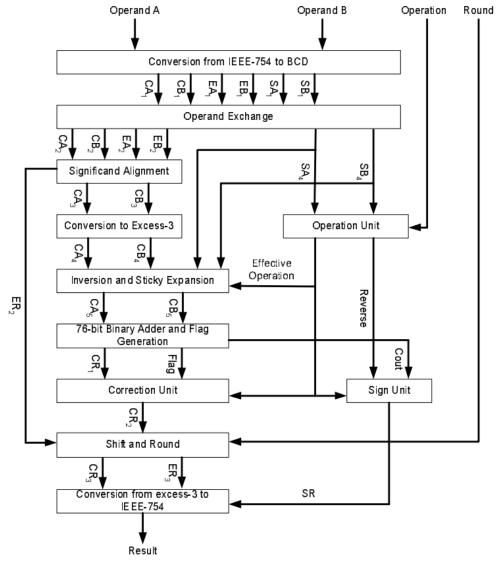



Multiply:



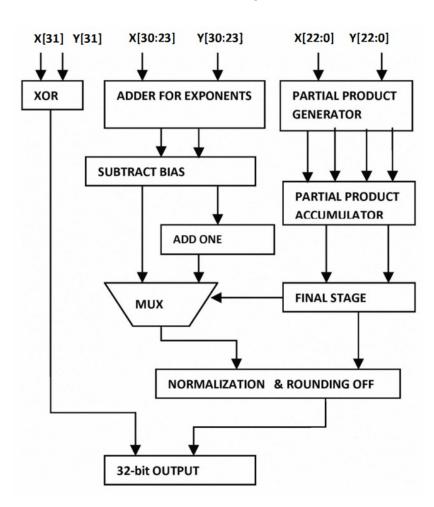

Sign: XOR

Exponent: Add

Mantissa: Multiply

Jain, Anna, et al. "FPGA design of a fast 32-bit floating point multiplier unit." 2012 International Conference on Devices, Circuits and Systems (ICDCS). IEEE, 2012.





Numbers Arithmetic Circuits

### Floating Point ALU supports +-\*/

#### **RISC-V floating-point assembly language**

Category	Instruction	Example	Meaning	Comments
Arithmetic	FP add single	fadd.s f0, f1, f2	f0 = f1 + f2	FP add (single precision)
	FP subtract single	fsub.s f0, f1, f2	f0 = f1 - f2	FP subtract (single precision)
	FP multiply single	fmul.s f0, f1, f2	f0 = f1 * f2	FP multiply (single precision)
	FP divide single	fdiv.s f0, f1, f2	f0 = f1 / f2	FP divide (single precision)
	FP square root single	fsqrt.s f0, f1	f0 = √f1	FP square root (single precision)
	FP add double	fadd.d f0, f1, f2	f0 = f1 + f2	FP add (double precision)
	FP subtract double	fsub.d f0, f1, f2	f0 = f1 - f2	FP subtract (double precision)
	FP multiply double	fmul.d f0, f1, f2	f0 = f1 * f2	FP multiply (double precision)
	FP divide double	fdiv.d f0, f1, f2	f0 = f1 / f2	FP divide (double precision)
	FP square root double	fsqrt.d f0, f1	f0 = √f1	FP square root (double precision)
Comparison	FP equality single	feq.s x5, f0, f1	x5 = 1 if f0 == f1. else 0	FP comparison (single precision)
	FP less than single	flt.s x5, f0, f1	x5 = 1 if f0 < f1, else 0	FP comparison (single precision)
	FP less than or equals single	fle.s x5, f0, f1	x5 = 1 if f0 <= f1, else 0	FP comparison (single precision)
	FP equality double	feq.d x5, f0, f1	x5 = 1 if f0 == f1, else 0	FP comparison (double precision)
	FP less than double	flt.d x5, f0, f1	x5 = 1 if f0 < f1, else 0	FP comparison (double precision)
	FP less than or equals double	fle.d x5, f0, f1	x5 = 1 if f0 <= f1, else 0	FP comparison (double precision)
Data transfer	FP load word	flw f0, 4(x5)	f0 = Memory[x5 + 4]	Load single-precision from memory
	FP load doubleword	fld f0. 8(x5)	f0 = Memory[x5 + 8]	Load double-precision from memory
	FP store word	fsw f0, 4(x5)	Memory[x5 + 4] = f0	Store single-precision from memory
	FP store doubleword	fsd f0, 8(x5)	Memory[x5 + 8] = f0	Store double-precision from memory





- Memory
- Arithmetic Unit
  - Number Systems
    - Integer
    - Fixed-Point
    - Floating-Point
  - Arithmetic
  - Circuits & Implementation